

(DCS 222)

B.Tech. DEGREE EXAMINATION, MAY - 2015

(Examination at the End of Second Year)

COMPUTER SCIENCE

Paper - II : Circuit Theory

Time : 3 Hours

Maximum Marks : 75

Answer question No.1 compulsory

(15)

Answer ONE question from each unit


(4 × 15 = 60)

- 1) a) Write about KVL.
- b) When 'n' capacitors are connected :
- i) What is the effective resistance in series combination.
- ii) What is the effective resistance in parallel combination.
- c) State Thevenin's theorem and Norton's theorem.
- d) Define peak factor, crest factor, form factor.
- e) Give the differences between series and parallel resonance.
- f) Define quality factor and give relation between quality factor and bandwidth.
- g) What are the advantages of three phase system.
- h) What is a balanced system.
- i) What is meant by source transformation technique.
- j) Give the expression for energy stored in capacitor & inductor.

UNIT - I


- 2) a) Write about Mesh analysis.

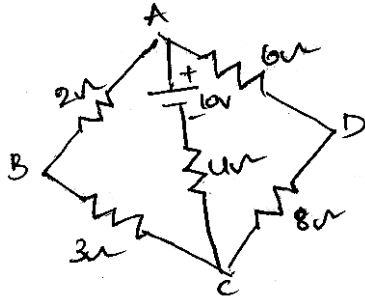- b) Calculate current in each element of the circuit.




OR

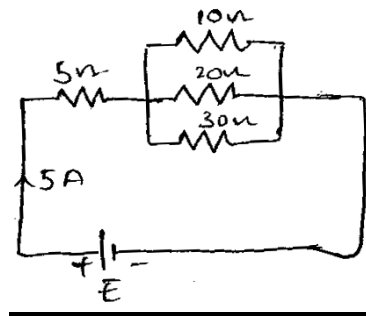- 3) a) Write about Nodal analysis.
 b) In the circuit shown in figure the current is 5 A. Calculate power consumed by 5Ω resistor. Also determine current through 10 Ω resistor and the supply voltage E.



UNIT - II

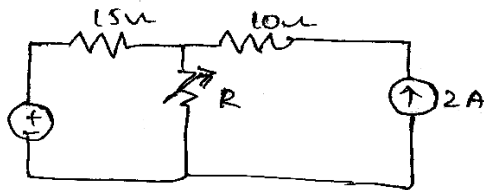- 4) a) Define maximum power transfer theorem.
 b) Find value of R for maximum power transfer. Also calculate the maximum power.



OR

- 5) Derive the expression for response when RC series circuit is excited by a AC source.

UNIT - III

- 6) a) For a π – connected resistive network, compute short circuit z -parameters.
 b) A series RLC circuit consists of $R = 50 \Omega$, $L = 20 \mu\text{H}$ and $C = 10 \mu\text{F}$. The applied voltage is 100V. Find (i) W_o (ii) Q_o (iii) Bandwidth

OR

- 7) Derive the expression for resonant frequency and quality factor for series resonance.

UNIT - IV

- 8) a) What is polyphase system and write its advantages.
- b) For a star connected network, derive the relationship b/w line and phase values with the help of phasor diagram.

OR

- 9) a) Describe about generation of 3- ϕ voltages.
- b) Determine the active and reactive components of voltages in each phase of star connected 4400V, 3-phase s/m supplying 3500 kW at a power factor 0.65.

