

(DEC 212)

**B. Tech. DEGREE EXAMINATION, MAY - 2015**

**(Examination at the end of Second Year)**

**ELECTRONICS & COMMUNICATIONS**

**Paper - II : Circuit Theory**

**Time : 3 Hours**

**Maximum Marks : 75**

*Answer question No.1 compulsory*

*(10 × 1½ = 15)*


*Answer ONE question from each unit*

*(4 × 15 = 60)*

- 1) a) Define ideal Elements.
- b) Units of  $\phi$  & G.
- c) Define power.
- d) Write about KCL.
- e) Difference b/w mesh and nodal Analysis
- f) Relation b/w power, voltage & Current.
- g) State Reciprocity theorem.
- h) AVG and RMS value of sinusoidal waveforms.
- i) Relation b/w Bandwidth and Q – Factor.
- j) Advantages of three phase system.


**UNIT - I**

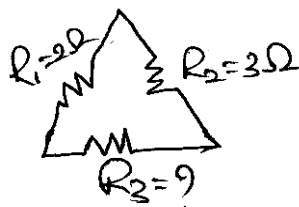- 2) a) Explain about the star to delta & delta to star.
- b) Find the R3 value.




OR

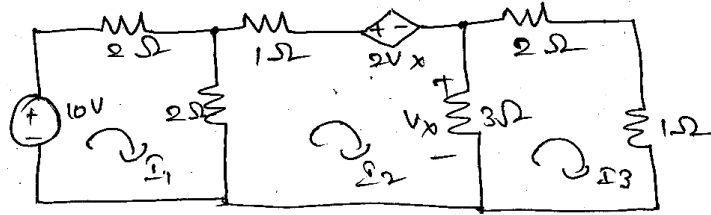- 3) a) Write about mesh analysis of circuits excited by independent and dependent sources.  
b) Solve the mesh currents of the circuits shown in fig .




UNIT - II

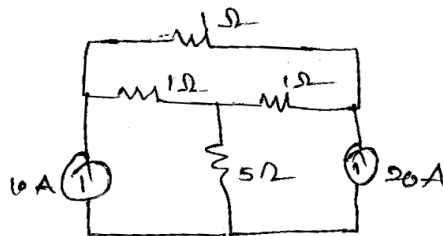- 4) a) State and prove the superposition theorem.  
b) Find the current in the 5Ω resistor of given fig. using superposition theorem.



OR

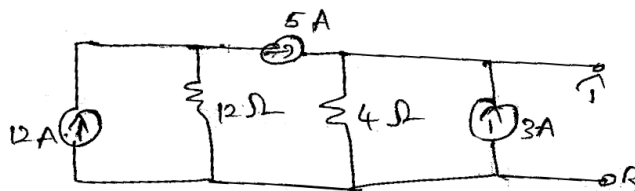- 5) Determine the Thevenin's & Norton's equivalent of the circuits shown in fig. 1 with respect to terminals A & B.



UNIT - III

- 6) Calculate the response of R, L iC series and parallel. Combination circuits to sinusoidal excitation.

OR


- 7) Explain about Series Resonance and derive the expression for resonant frequency & quality factor.

UNIT - IV

- 8) What is poly phase system & Explain its advantages and disadvantages. Explain its operation for 3phase sources and loads.

OR

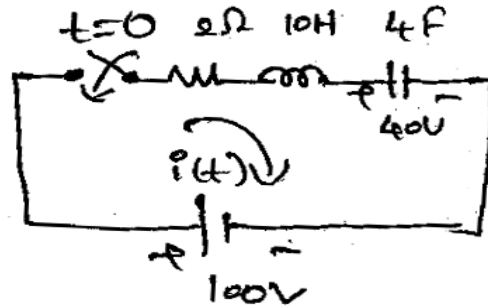- 9) In the RLC circuit of fig. the capacitor has an initial voltage of 40v, when the switch is closed at  $t = 0$ . Find an expression for the current  $i(t)$



❀❀❀❀