

(DEC 222)

B. Tech. DEGREE EXAMINATION, MAY - 2015

(Examination at the end of Second Year)

ELECTRONICS & COMMUNICATIONS

Paper - II : Electronic Circuits - I

Time : 3 Hours

Maximum Marks : 75

Answer question No.1 compulsory

Answer ONE question from each unit

- 1) a) Define miller's theorem
- b) Why h- parameter are not suitable at high frequencies?
- c) What are the applications rectifiers?
- d) List out characteristics of Darlington pair.
- e) What are advantages of RC coupling in multistage amplifier?
- f) List out characteristics of CS amplifier
- g) Compare BJT and FET amplifiers
- h) What is effect of bypass capacitor in CE amplifiers?
- i) Define Harmonic distortion

UNIT-I

- 2) a) Explain the operation of center tapped FWR. with circuit and necessary waveforms
- b) Design a filter for FWR circuit with LC filter to provide an output voltage of 10 volts with a load current of 200 mA and the ripple is limited to 2%

OR

- 3) a) With circuit and necessary waveforms explain the operation of Bridge Rectifier

- b) In a Bridge rectifier, the transformer is connected to 220 volts, 60 Hz mains and turns ratio of the step down transformer is 11:1. Assuming the diodes to be ideal, find
- voltage across the load
 - D.C current
 - PIV.

UNIT – II

- 4) a) Classify different types of amplifiers?
- b) The h-parameters of a CE amplifier are $h_{ie} = 1100\Omega$, $h_{fe}=50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 24\mu A/V$ and $R_s = 1k\Omega$ and $R_L = 10k\Omega$. Find the current and voltage gain, (with and without source resistance) input & output impedances

OR

- 5) a) Explain in detail different types of distortions in amplifier.
- b) Compare CE,CC and CB amplifier.

UNIT-III

- 6) a) Describe the emitter follower at high frequency and also derive the equation for higher cutoff frequency
- b) Write Short note Gain Bandwidth product

OR

- 7) a) Define and explain terms f_β and f_T .
- b) Derive the expression for CE short circuit current gain and explain the significance of f_T in hybrid π model.

UNIT-IV

- 8) a) Draw the circuit diagram of cascade amplifier and derive its overall voltage gain and Input impedance from its equivalent circuit.
- b) Discuss different coupling methods used in multistage amplifier

OR

- 9) a) Explain the small signal MOSFET circuit model.
- b) Draw and explain the CS amplifier with current source load.

