

**(DEC 415)**

**B. Tech. DEGREE EXAMINATION, MAY - 2015**

**(Examination at the end of Final Year)**

**ELECTRONICS AND COMMUNICATION ENGG.**

**Paper - V : VLSI Design**

**Time : 3 Hours**

**Maximum Marks : 75**

*Answer question No. 1 compulsory*

*(15)*

*Answer ONE question from each unit*

*(4 x 15 = 60)*

- 1) a) What are the advantages of FPGAs?
- b) Write the program structure of VHDL.
- c) What are the advantages of BiCMOS Technology?
- d) Draw the circuit diagram of CMOS inverter.
- e) Write an ENTITY of 4X1 MUX in VHDL.
- f) Write the expression for drain current in saturation region.
- g) Define logic synthesis.
- h) What is lithography technique?
- i) Write scaling factor of Gate capacitance.
- j) Compare CPLDs and FPGAs.

**Unit - I**

- 2) a) Short notes on advanced CMOS fabrication technologies.
- b) Write a short note on following :
- i) Figure of merit
- ii) Pass transistor

OR

- 3) a) Explain various regions of CMOS inverter transfer characteristics.  
b) Write short note Latch up in CMOS circuits.

**Unit – II**

- 4) a) Draw the layout for NMOS inverter circuit.  
b) Write short note wiring capacitances.

OR

- 5) a) Draw the stick diagram and layout of CMOS 2 input NOR gate.  
b) Explain Lambda ( $\lambda$ ) based design rules.

**Unit – III**

- 6) a) Construct an 8-bit Carry select adder Using adders and multiplexers.  
b) Draw the schematic and logic diagram for a single bit adder and explain its Operation with truth table.

OR

- 7) a) Compare the different types of CMOS subsystem Multipliers.  
b) Design logic for an ALU that can perform both logical and arithmetic operations.

**Unit – IV**

- 8) a) Implement of full adder using PLA.  
b) Describe behavioral design elements with examples.

OR

- 9) a) Explain about anti fuses used in FPGAs.  
b) Write a program in VHDL for an 2X4 Decoder in behavioral and structural style.