

Code : 031505

B.Tech 5th Semester Exam., 2014

NETWORK THEORY

Time : 3 hours

Full Marks : 70

Instructions :

- (i) All questions carry equal marks.
 (ii) There are **NINE** questions in this paper.
 (iii) Attempt **FIVE** questions in all.
 (iv) Question No. 1 is compulsory.

1. Choose the correct answer from any *seven* of the following :

(a) In the circuit shown in Fig. 1

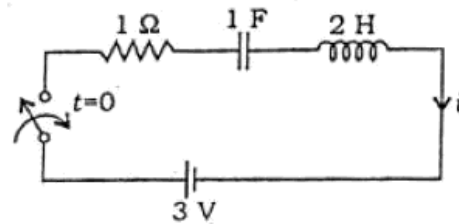


Fig. 1

the current i and the rate of change of current $\frac{di}{dt}$ at $t=0$ are given by

- ~~(i) 0, 0~~
 (ii) 1, 2
 (iii) 0, 3
 (iv) None of the above

(b) For critical damping the value of C in the circuit, shown in Fig. 2

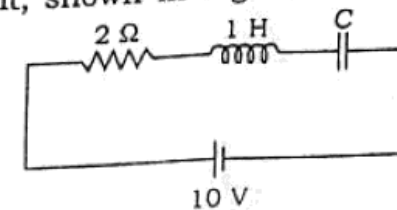


Fig. 2

is

- (i) 2 F (ii) 1 F
 (iii) 1.5 F (iv) 3 F

(c) The condition for reciprocity in h -parameters is

- (i) $h_{12} = h_{21}$ (ii) $h_{12} = -h_{21}$
 (iii) $h_{11} = h_{22}$ (iv) $h_{12} = h_{22}$

(d) The Z_{11} and Z_{22} parameters of the network shown in Fig. 3

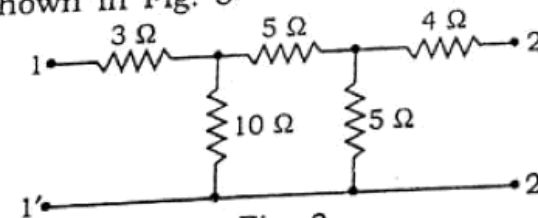


Fig. 3

are

- ~~(i) 8 Ω, 7.75 Ω~~
 (ii) 13 Ω, 9 Ω
 (iii) 12 Ω, 8.5 Ω
 (iv) None of the above

- (e) The cut-off frequencies of constant- k filters of all types are represented by

(i) $\frac{Z_1}{4Z_2} = 1$

(ii) $\frac{Z_1}{4Z_2} = 0$

~~(iii) $\frac{Z_1}{4Z_2} = -1$~~

- (iv) None of the above

- (f) The Cauer form-II of a reactive network synthesis is the successful removal of

(i) poles at infinity

~~(ii) zero at infinity~~

(iii) poles at origin

(iv) zero at origin

- (g) If $F_1(s)$ and $F_2(s)$ are two positive real functions, then the function which is always positive real is

(i) $F_1(s)F_2(s)$

~~(ii) $\frac{F_1(s)}{F_2(s)}$~~

(iii) $\frac{F_1(s)F_2(s)}{F_1(s) + F_2(s)}$

(iv) $F_1(s) - F_2(s)$

- (h) For a given network, the reduced incidence matrix is given as

$$\begin{bmatrix} & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 1 & 1 & 0 & 0 & 1 & 0 & -1 & 1 \\ & -1 & -1 & 1 & 0 & 0 & 0 & 0 \\ & 0 & 1 & 0 & -1 & 1 & 0 & 0 \end{bmatrix}$$

The parallel branches in the graph are

(i) 1 and 2

~~(ii) 2 and 3~~

~~(iii) 6 and 7~~

(iv) None of the above

- (i) Which one of the following statements is correct?

A tree in a network is a connected graph containing

~~(i) all the nodes only~~

(ii) all the branches only

(iii) all the branches and nodes

(iv) all the branches but no closed path

- (j) For a transfer function, $H(s) = \frac{P(s)}{Q(s)}$, where

$P(s)$ and $Q(s)$ are polynomials in s ,

(i) the degree of $P(s)$ is always greater than the degree of $Q(s)$

~~(ii) the degree of $P(s)$ and $Q(s)$ are the same~~

(iii) the degree of $P(s)$ is independent of the degree of $Q(s)$

(iv) the maximum degree of $P(s)$ and $Q(s)$ differ at the most by one

2. For the circuit shown in Fig. 4, find $i_L(t)$ and $v_C(t)$ for $t > 0$:

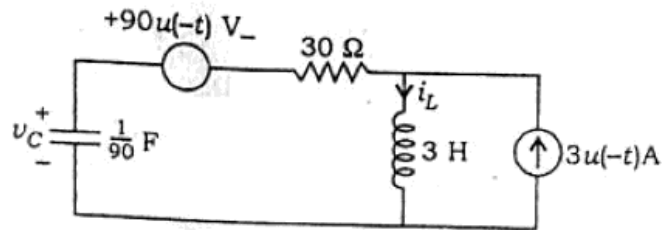


Fig. 4

3. (a) A one-port network has a coil of inductance L and resistance R shunted by a capacitance C . If poles and zeros of driving-point impedance $Z(s)$ of this network are as poles at $-1 \pm j\sqrt{3}$ and zero at -2 with $Z(s)$ at $s=0$ equal to 2, find R , L and C .

- (b) For the network shown in Fig. 5, find the transfer admittance function $Y_{12}(s)$:

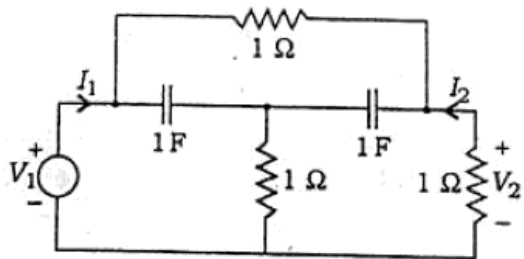


Fig. 5

4. For the network shown in Fig. 6, determine Y-parameters :

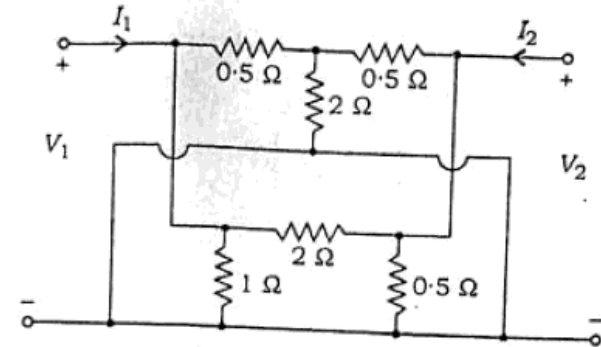


Fig. 6

5. For the network shown in Fig. 7, draw the graph find the fundamental loop matrix taking branches 2, 4, 5 as tree branches and write the loop impedance matrix and loop equations :

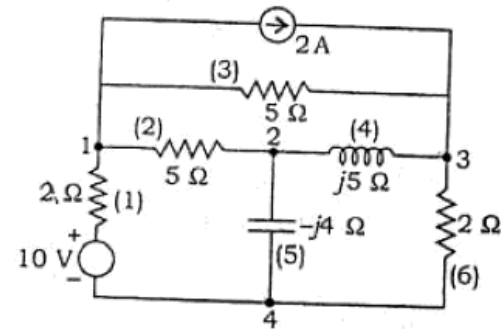


Fig. 7

6. If a constant- k high-pass filter has cut-off frequency of 10 kHz and the nominal impedance R_0 is 700 Ω , design the T - and π -sections of the filter. Determine its characteristic impedance phase constant at 25 kHz and attenuation at 8 kHz.

7. Synthesize the following impedance function in Foster Form-II and Cauer Form-I :

$$Z(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

8. (a) The switch in the circuit shown in Fig. 8 is opened at $t=0$. Determine $v(t)$ for $t > 0$:

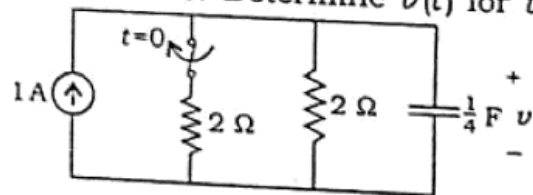


Fig. 8

- (b) Derive reciprocity condition for two-port network in terms of hybrid parameters.
9. (a) The matrix A given below is a reduced incidence matrix of a graph. Draw the graph :

Nodes	Branches					
	1	2	3	4	5	6
1	1	0	0	-1	0	1
2	-1	0	1	0	1	0
3	0	1	-1	0	0	0

- (b) Write the properties of L - C immittance function.
