

**B.E. FULL TIME END SEMESTER EXAMINATIONS, NOV / DEC 2012**  
**II SEMESTER REGULATIONS R 2008**  
**EC 9152 CIRCUIT ANALYSIS**

Time: 3 Hours

Max Mark : 100

**ANSWER ALL QUESTIONS**

**PART-A**



(10X2=20 marks)

1. A  $10\ \Omega$  resistor is in series with a parallel combination of two resistors of  $15\ \Omega$  and  $5\ \Omega$ . If the constant current in the  $5\ \Omega$  resistor is 6 amperes, what total power is dissipated in the three resistors.
2. A total voltage of 5 volts drops across two resistors in series. If the resistor values are  $R_1 = 10\ \Omega$  and  $R_2 = 40\ \Omega$ , determine the voltage drop across each resistor.
3. Define duality and draw dual of series resonant circuit.
4. Three  $90\ \Omega$  resistors are connected in a delta connection. Determine wye equivalent.
5. Define power factor.
6. Determine the value of resistance and capacitive reactance of two element series circuit which has the applied voltage of  $70\ 30^\circ\ \text{V}$  and current of  $19\ 75^\circ\ \text{A}$ .
7. Define quality factor.
8. Draw the variation of current with respect to frequency of a series RLC circuit.
9. Define coefficient of coupling.
10. What is tie-set?

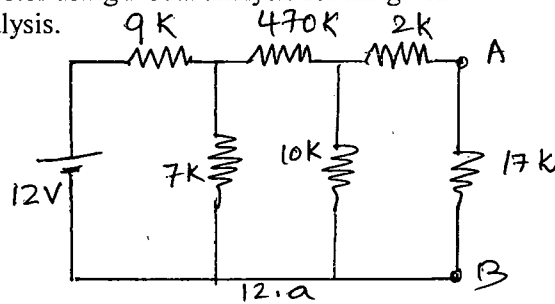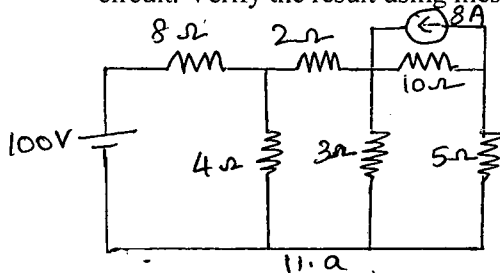**PART-B**

(5X16=80 marks)


- 11a. Determine voltage drop across  $10\ \Omega$  resistor using Nodal analysis for the given circuit. Verify the result using mesh analysis.




- 12 a. Determine the Norton's equivalent circuit at terminals AB of the network given. Verify the equivalent circuit using Thevenin's theorem.

OR

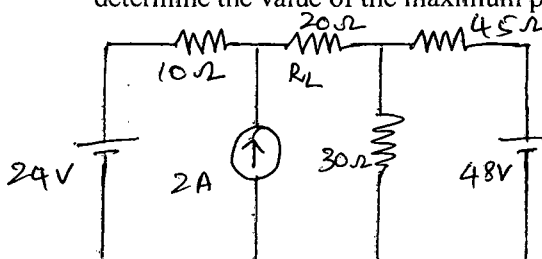- b.i) Use Superposition theorem to find the power dissipated by the  $R_L$  resistor in the given circuit.
- ii) Find the value of  $R_L$  for which the source delivers maximum power to the load and determine the value of the maximum power.



12. b. (i)

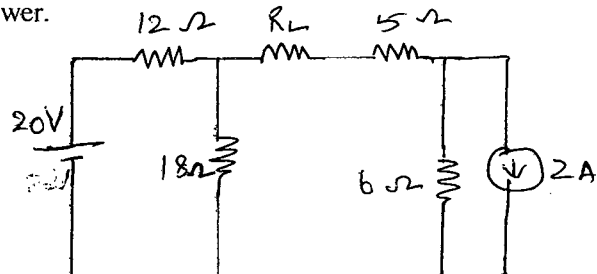


12. b. (ii)


- 13a.i) A series circuit of  $R = 25$  ohms and  $L = 0.01$  H is to be used at frequencies of 100, 500 and 1000 hertz. Find the impedance at each of these frequencies.
- ii) Determine the power triangle for a given circuit with applied voltage of  $v = 150 \sin(\omega t + 10^\circ)$  volts and a resulting current  $i = 5 \sin(\omega t - 50^\circ)$  amperes.

OR

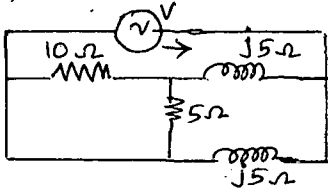- b.i) Determine the effective voltage of the source which results in a power of 100 watts in the 5 ohms resistor using mesh analysis.
- ii) Determine the current through  $j10$  ohm using nodal analysis.



13.b.(i)

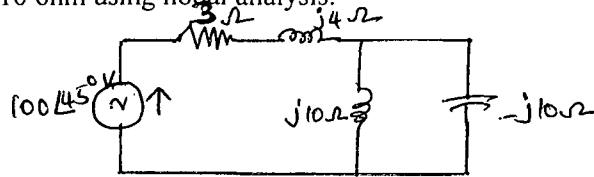


13.b.(ii)


- 14a. A voltage  $v(t) = 10 \sin \omega t$  is applied to a series RLC circuit. At the resonant frequency, the maximum voltage across the capacitor is found to be 500V. The bandwidth is 400 rad/sec and the impedance at resonance is 100 ohm. Derive and determine the resonant frequency, upper and lower limits of the bandwidth and the values of L and C of the circuit.

OR

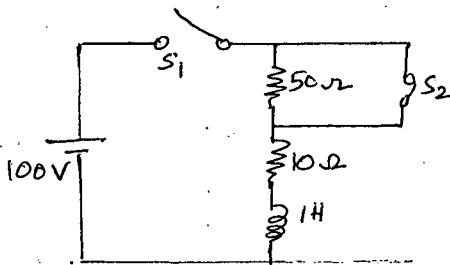- b.i) In the circuit shown, the switch  $S_1$  is closed at  $t = 0$  and switch  $S_2$  is opened at  $t = 0.2$  seconds. Find the transient current expressions for the two intervals.
- ii) Two impedances  $Z_1 = 20 + j10$  and  $Z_2 = 10 - j30$  are connected in parallel and this combination is connected in series with  $Z_3 = 30 + jX$ . Find the value of X which will produce resonance



14.b.(i)

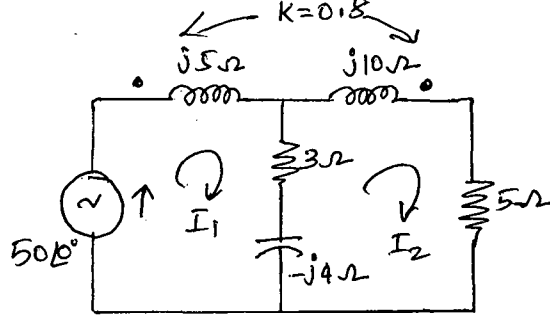

15.a

- 15a. Determine the voltage across 5 ohm resistor of the coupled circuit shown.

OR

- b. Explain how incidence matrix is derived from a graph with suitable example and express the branch current in terms of loop current using tie-set matrix.

-----