

[06 - 2111]

II/IV B.E. DEGREE EXAMINATION.

First Semester

Electrical and Electronics Engineering

Electrical Measurements

(Common with MS Electrical and
Electronics Engineering)

(w.e.f. admitted batch of 2006-2007)

Time : Three hours

Maximum : 70 marks

Answer question No.1 and any other FOUR questions.

All questions carry equal marks.

1. (a) Define the terms accuracy and precision.
- (b) What is standard cell and standard resistance?
- (c) What type of damping used in MI type instruments?
- (d) List the factors which will effect the resistance of an earth electrode.

- (e) Write the advantages of Anderson's Bridge.
- (f) What is leakage factor? List the method to determine it?
- (g) List out the advantages of coordinates type potentiometer.
2. (a) Define the terms (i) Repeatability (ii) Accuracy (iii) Precision (iv) Static sensitivity (v) Resolution (vi) Linearity.
- (b) Explain the principle and working of a permanent magnet moving coil type instruments and derive the expression for net torque and angle.
3. (a) Explain the construction of dynamometer instruments.
- (b) Write about frequency meter and discuss its working principle.
4. (a) Draw the circuit of a Kelvin's Double Bridge used for measurement of low resistance. Derive the condition for balance.
- (b) Explain the loss of charge method for measurement of insulation resistance of cable.

5. (a) Draw and explain campbell's bridge with neat sketch.
- (b) Describe working of a low voltage schering bridge. Derive the equation for capacitance and dissipation factor. Draw the phasor diagram of the bridge under conditions of balance.
6. (a) Describe a method of experimental determination of flux density in a specimen of magnetic material using ballastic galvanometer.
- (b) Describe the method for determination of B-H curve of a magnetic material using methods of reversal.
7. (a) Write about Fisher square for measurement of iron loss, briefly.
- (b) Draw the circuit diagram of a crompton's potentiometer and explain its working.
8. (a) Describe how high currents and voltage are measured with the help of instrument transformers? Describe the advantages.
- (b) Explain the effect of secondary burden on the ratio and phase error of current transformers.