

[06 – 2203]

II/IV B.E. DEGREE EXAMINATION.

Second Semester

Electrical and Electronics Engineering

ANALOG ELECTRONIC CIRCUITS

(Common with Electronics and Communication  
Engineering and EIE)

(Effective from the admitted batch of 1999–2000 and  
after batches)

Time : Three hours

Maximum : 70 marks

Question no. 1 is compulsory.

Answer any FOUR questions from the remaining.

All questions carry equal marks.

1. (a) What is the need of a difference amplifier?
- (b) What is the effect of—ve feedback on gain?
- (c) Write the advantages of crystal oscillators.
- (d) What are the advantages of push pull amplifier?

7. (a) Draw the block diagram of operational amplifier. Explain in detail.

(b) A differential amplifier has a differential gain ( $A_d$ ) of 100, the input voltages applied are  $V_1 = 1 \text{ mV}$  and  $V_2 = 0.9 \text{ mV}$ .

Calculate the output voltage for

(i)  $\text{CMRR} = 100$

(ii)  $\text{CMRR} = 1000$

(iii)  $\text{CMRR} = 10000$ .

8. (a) Describe the logarithmic amplifier with neat sketches.

(b) Design a weighted summer using Op-Amp that provides  $V_0 = 2V_1 + V_2 - 4V_3$ .

---

- (e) What is the need of heat sinks in power amplifiers?
- (f) List the ideal characteristics of Op-Amp.
- (g) What is CMRR? Define.
2. (a) With neat diagram, explain the working of 2-stage RC coupled amplifier
- (b) Explain high frequency operation of FET and derive the expression for gain bandwidth product with necessary diagrams.
3. (a) Find the input and output resistance of a amplifier that employs voltage series feedback.
- (b) An amplifier with —ve feedback has a voltage gain of 120. It is found that without feedback, an input signal of 60 mV is required to produce a particular output, where as with feedback the input signal must be 0.5 V to get the same output. Find the  $A_V$  and  $\beta$  of the amplifier. (4)
- (c) Mention the advantages of — ve feedback. (3)

4. (a) What are the types of LC tuned oscillators Explain any one with neat figure and with necessary equations.
- (b) In a Harpits oscillator  $L_1 = 5\mu H$ ,  $L_2 = 15\mu H$  and  $C = 0.01\mu F$ . Calculate :
- (i) Frequency of oscillations
- (ii) If 'C' is doubled, find the new frequency.
5. (a) Explain about class AB power amplifier with neat sketches.
- (b) Calculate the harmonic distortion components of an output signal having fundamental amplitude of 2.5 V, 2<sup>nd</sup> harmonic amplitude of 0.25V and 3<sup>rd</sup> harmonic amplitude 0.1 V and 4<sup>th</sup> harmonic amplitude 0.05V and also calculate the total harmonic \* distortion for the amplitude component given above.
6. (a) What is the use of using transformers in a tuned circuit?
- (b) What is meant by stragger tuning? Explain.
- (c) What are the differences between single and stragger tuning?