

[06 - 3218]

III/IV B.E. DEGREE EXAMINATION.

Second Semester

Electrical and Electronics Engineering

POWER ELECTRONICS

(Effective from the admitted batch of 2006-2007)

Time : Three hours

Maximum : 70 marks

Question No. 1 is compulsory.

Answer any FOUR from the remaining.

All questions carry equal marks.

1. (a) Describe holding current, latching current as applicable to an SCR with the help of its static V-I characteristic.
- (b) Explain in brief the prime requirement of a trigger pulse transformer.
- (c) Write a brief note on string efficiency of SCRs.
- (d) Justify the statement "Freewheeling diode improves the power factor of the system".
- (e) How are inverters classified?

- (f) Draw the schematic of step-up chopper.
 - (g) Explain the basic principle of operation of a cycloconverter with a neat equivalent circuit diagram.
- 2.
- (a) Draw the turn off characteristic of an SCR and explain the mechanism of turn-off.
 - (b) What are the different methods for turning off an SCR? Explain all methods in detail.
- 3.
- (a) Draw and explain the necessity of static and dynamic equalizing circuit for series connected SCRs.
 - (b) Draw and explain circuit diagram for the synchronized UJT triggering.
- 4.
- (a) Explain with the help of neat power diagram and associated waveforms, the operation of a single-phase half wave controlled converters with (i) resistive load (ii) inductive load.
 - (b) Explain the effect of source inductance on the performance of a three-phase fully controlled bridge converter.

5. (a) Explain the following performance parameters of inverters.
- (i) Harmonic factor of n^{th} harmonic
 - (ii) Total harmonic distortion
 - (iii) Distortion factor
 - (iv) Lowest order harmonic.
- (b) Compare between voltage source and current source inverters.
6. (a) Explain the time ratio control, current limit control and control strategies used for chopper.
- (b) With the help of circuit diagram, explain the working of step-up chopper.
7. (a) Describe the basic principle of working of a single-phase to single-phase cycloconverter for continuous conduction for a bridge type cycloconverter.
- (b) Draw and explain the control circuit block diagram for a cycloconverter with non circulating current mode.
8. (a) Explain the safe operating areas of IGBT.
- (b) How does a GTO differ from a conventional thyristor? Give its circuit symbol.