

[06 - 4113]

IV/IV B.E. DEGREE EXAMINATION.

First Semester

Electrical and Electronics Engineering

POWER SYSTEM ANALYSIS AND STABILITY

(Effective from the admitted batch of 2004-2005)

Time : Three hours

Maximum : 70 marks

Answer question No. 1 and any FOUR from the rest.

All questions carry equal marks.

1. (a) Obtain the value of the per unit impedance when the 3-phase base quantities are given.
- (b) Mention any two reasons in favour of N-R method compared to G-S method of load flow solution.
- (c) Define the following terms clearly w.r.to a synchronous machine.
 - (i) Quadrature axis transient reactance
 - (ii) Quadrature axis subtransient reactance.

- (d) Determine the zero sequence component voltage of the unbalanced 3-phase voltages as given below for the A, B, C phase sequence.

$$V_A = 200 \angle 0^\circ \text{ volts ; } V_B = 200 \angle 230^\circ \text{ volts and}$$

$$V_C = 200 \angle 100^\circ \text{ volts}$$


- (e) Define : Steady state stability and transient stability of power systems.
- (f) Show that L - L fault, $I_{a0} = 0$ and $I_{a1} = -I_{a2}$. Mention the reason for $I_{a0} = 0$ in this type of fault.
- (g) (i) Define single-line diagram w.r.to a power system.
(ii) Write the swing equation.

2. (a) Prove that for a transformer, the p.u. value of impedance will be the same when referred to either side of the transformer.
- (b) Obtain the p.u. impedance diagram of the power system shown in the figure below. Choose the base quantities as 15 MVA and 33 kV.


Transformers T_1 and T_2 : 15 MVA, 33/11 kV,
 $X = 15\Omega$ referred to HV.

Transmission line : 20 ohms/phase

Load : 40 mW, 6.6. kV, 0.85 lagging p.f.

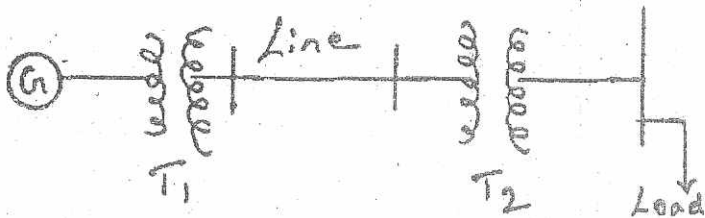

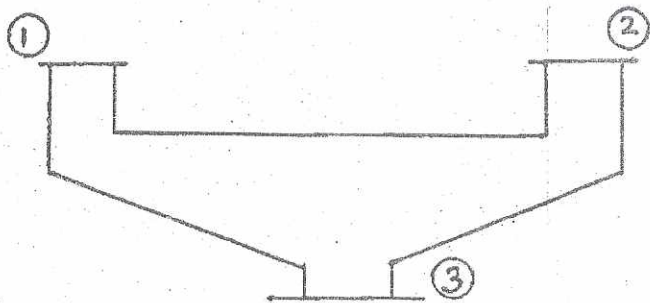3. (a) Develop the load equations and explain Gauss-Seidal method of solving them for a 5-bus system. Use flow chart.
- (b) Obtain the Bus-impedance matrix for the 3-bus system shown in the figure below.



$$Z_{1-2} = 0.008 + j 0.24; \quad Z_{13} = 0.002 + j 0.06$$

$$Z_{23} = 0.06 + j 0.18.$$

All are p.u. values.

4. (a) Compare G-S, N-R and fast decoupled load flow methods with respect to
- (i) Number of equations
 - (ii) Memory and
 - (iii) Time for iteration.
- (b) In a 2-bus power system with bus 1 as slack bus with $V_1 = 1.02 \angle 0^\circ$ p.u and $P_2 = 3.0$ p.u; $Q_2 = 0.8$ p.u and $Z_2 = 0.025 + j0.045$ p.u. Using G - S method, determine V_2 after two iterations.
5. (a) Describe the various types of current limiting reactors used in power systems.
- (b) Two 50 MVA, 50 Hz, 11 kV alternators with subtransient reactance $X'' = 0.1$ p.u and a transformer of 40 MVA, 11/66 kV and reactance of 0.08 p.u are connected to a bus A. Another generator rated 60 MVA, 11 kV with a reactance of 0.12 p.u is connected to bus B. Both A and B are interconnected through a reactor of 80 MVA, 20% reactance. If a 3-phase fault occurs on the H.V. side of the transformer, calculate the current fed into the fault and fault MVA.

6. (a) A line-to-line fault occurs at the terminals of an unloaded synchronous generator. Derive the interconnection of sequence networks and expressions for the pre-fault currents in the machine.
- (b) A 20 MVA, 11 kV, Star connected generator has positive, negative and zero sequence reactances of 25%, 35% and 100% respectively. The neutral is earthed through a reactance of 8%. When the generator is unloaded, a double line to ground fault occurs in phases b and c. Calculate the fault currents in all the three phases. Assume the voltage generated to be 11 kV phase sequence is abc.
7. (a) Derive the swing equation of a synchronous machine. The steady state limit of a power system is 100 mW. A generator with constant excitation is supplying 50 mW to the system. Estimate the maximum possible sudden increase in generator output without causing instability.
- (b) Mention various methods of which transient stability can be improved.

8. Write short notes on the following :

- (a) Data received for load flow studies
 - (b) Critical clearing time
 - (c) Phase shift in delta/star transformers.
-