

# B. Tech Second Year : 3<sup>rd</sup> Semester

# Electronic Devices & Circuits, Jan., 2012

(FOR 3EC2 BRANCH OF ENGINEERING)

**Times : 3 Hours**                      **Min. Passing Marks : 24**                      **Total Marks : 80**

*Attempt overall five questions in all. Schematic diagrams must be shown wherever necessary. Any data you feel missing may suitably be assumed and stated clearly.*

### Unit-I

1. (a) Describe the conductivity and mobility for intrinsic semiconductor. [8]
- (b) Find the conductivity of intrinsic germanium at 300°K. If donor type impurity is added to the extent of 1 impurity atom in  $10^7$  germanium atoms, find the conductivity. Given that  $n_i$  at 300°K is  $2.5 \times 10^{13}/\text{cm}^3$  and  $\mu_n$  and  $\mu_p$  of germanium are 3800 and 1800  $\text{cm}^2/\text{v-s}$  respectively. [8]

**OR**

1. (a) What is Hall effect, how it is useful for measuring various parameters of semiconductor? [8]
- (b) What do you mean by Fermi level? Derive the expression for fermi level and sketch the position in case of intrinsic, p-type and n-type semiconductor. [8]

### Unit-II

2. (a) Draw and explain the working of DC inserter circuit. [8]
- (b) What do you mean by clipper circuit? The sinusoidal input given to below circuit, what will be the output : Fig.1? [8]

 


Fig. 1

**OR**

2. (a) Describe the importance of load line concept used in electronic circuits. [8]
- (b) Explain the effect of negative resistance region in the V-I characteristic of UJT, also give its applications. [8]

### Unit-III

3. (a) Explain Ebers-Moll model of transistor. [8]

- (b) Draw and explain the working of transistor as an amplifier. [8]

**OR**

3. (a) Write the steps for testing of transistors by digital multimeter.
  - (i) lead identification (base, collector, emitter)
  - (ii) type of transistor (npn or pnp)
  - (iii) it is good or not. [10]
- (b) Write short notes on stabilization techniques for transistor circuit used for different applications. [6]

### Unit-IV

4. (a) It is required to operate the JFET shown in fig. 2 at  $V_{GS} = -1\text{V}$ ,  $V_{DS} = 4\text{V}$  and  $I_{DS} = 1\text{mA}$ . Determine:
  - (i) value of  $R_D$  and  $R_S$
  - (ii) voltage gain
  - (iii) Input and output resistance

 


Fig. 2

- (b) Derive various parameters of JFET soft bias configuration useful in using different applications. [8]

**OR**

4. (a) Draw and explain the construction and operation of enhancement MOSFET. [8]
- (b) Write various techniques used for handling MOSFET in laboratory. [8]

### Unit-V

5. Write short notes on the following : (any two)
  - (a) Role of bootstrapping in darlington pair
  - (b) Emitter follower
  - (c) Cascading transistor amplifiers. [16]