

4E4120

Roll No. _____

Total No of Pages: 3

4E4120

B. Tech. IV Sem. (Main/Back) Exam., June/July-2014

Electronics Instrumentation & Control Engg.

4E11A Analog Electronics

Common with EE, EX, EC & EI

Time: 3 Hours

Maximum Marks: 80

Min. Passing Marks: 24

Instructions to Candidates:-

*Attempt any **five** questions, selecting **one** question from each unit. All Questions carry **equal** marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly.*

Units of quantities used/ calculated must be stated clearly.

Use of following supporting material is permitted during examination.

1. _____

2. _____

UNIT-I

Q.1. (a) Discuss with the help of a circuit example, the purpose of providing (i) negative feedback (ii) positive feedback in amplifiers. [8]

(b) A negative feedback of $\beta = 0.002$ is applied to our amplifier of gain 1000. Calculate the change in overall gain of the feedback amplifier if the internal amplifier is subjected to a gain reduction of 15%. [8]

OR

Q.1. (a) Show that the negative feedback in amplifiers increases the bandwidth and improves signal to noise ratio. [8]

- (b) Draw and explain the current shunt feedback. [8]

UNIT-II

Q.2. (a) State the Barkhausen conditions for an electronic system to oscillate with feedback. [8]

- (b) Draw the circuit diagram of a colpitts oscillator and explain its working. [8]

OR

Q.2. (a) Draw the circuit diagram of an R-C phase shift oscillator and obtain an expression for its frequency of oscillation. [8]

- (b) Differentiate between the monostable and bistable multivibrator. [8]

UNIT-III

Q.3. (a) Explain how would you arrive at the hybrid - π equivalent circuit model in CE configuration at high frequencies. Explain the different parameters involved in the circuit. [8]

- (b) A CE – connected amplifier has $C_{cb} = 5\text{pF}$, $C_{be} = 12\text{pF}$, $h_{fe} = 100$, $h_{ie} = 1.5\text{ k}\Omega$. Determine input capacitance to the circuit for a circuit collector resistance of 12Ω . [8]

OR

Q.3. (a) Draw the circuit of emitter follower at high frequencies and explain its working. [8]

- (b) A transistor with alpha cut-off frequency = 5 MHz and h_{fe} or $\beta = 50$ is used in a CE configuration. When connected to an amplifier, it has stray capacitance of 80 pF at the output terminals. Determine the upper 3dB frequency when

(i) $R_L = 10\text{k}\Omega$ and (ii) $R_L = 100\text{k}\Omega$ [8]

UNIT-IV

- Q.4. (a) What is parallel resonances? What are its features? How is it different from series resonances? [8]
- (b) Explain the reasons for potential instability in tuned amplifiers. [8]

OR

- Q.4. (a) Draw the circuit diagram of a collector tuned amplifier and derive expressions for the voltage gain at the tuned frequency and bandwidth. [8]
- (b) Explain in brief the advantage of using double – tuned circuit over a single tuned circuit. Draw the circuit diagram of double tuned amplifier and its frequency response. [8]

UNIT-V

- Q.5. (a) What is a power amplifier? In what respects does it differ from a voltage amplifier? Why heat sink are needed. [8]
- (b) Explain collector efficiency, distortion and power dissipation. [8]

OR

- Q.5. (a) Prove that for class B push-pull power amplifier the theoretical conversion efficiency is 78.5% and power dissipation capability of each transistor used shall be at least 0.2 times the maximum power output of the amplifier. [8]
- (b) Draw the circuit of class D and class E amplifier and their application. [8]

-----X-----X-----