

**3E1481**

Roll No. : \_\_\_\_\_

Total Printed Pages : **3****3E1481****B.Tech. (Sem. III) (Main/Back) Examination, February - 2010**  
**Electrical Engineering**  
**(3EE1 Power Electronics - I)**Time : **3 Hours**][Total Marks : **80**[Min. Passing Marks : **24**

*Attempt **five** questions in all. Schematic diagrams must be shown wherever necessary. Any data you feel missing may suitably be assumed and stated clearly.*

Use of following supporting material is permitted during examination.  
(Mentioned in form No. 205)

1. \_\_\_\_\_ **Nil** \_\_\_\_\_ 2. \_\_\_\_\_ **Nil** \_\_\_\_\_

1 (a) Explain the formation of depletion region in an open circuited P-N junction. 8

(b) Derive the expression for diffusion capacitance and show that diffusion capacitance is directly proportional to diode current I. 8

**OR**

1 (a) Draw the equivalent circuit and explain characteristics of varactor diode. 8

(b) Explain the operation of photo-diode and given its applications. 8

2 (a) Draw and explain Bridge-rectifier ckts. with waveforms. 8

(b) Prove that the maximum rectification efficiency of full-wave rectifier is 81.2%. 8

**OR**


2 (a) Sketch the output waveform of the following diode ckt. when  $V_i = 5 \sin 200 \pi t$  is applied to input

3E1481]



1

[Contd...

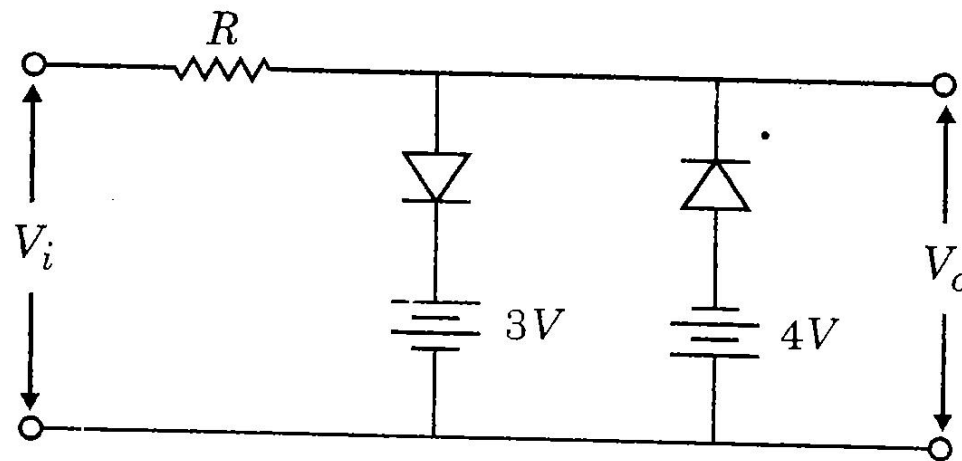

- (b) Draw and explain the ckt. of a voltage doubler and voltage quadruples. 8

8

- 3 (a) For a pnp transistor biased in active region indicate and discuss the various electron and hole current component crossing the junction. 8

8

- (b) Explain :

- (i) Diode compensation for  $V_{BE}$   
(ii) Thermistor compensation.

8

OR

- 3 (a) Explain the phenomenon of base width modulation. 8

8

- (b) Explain the function of a transistor as a switch. 8

8

- 4 (a) With the help of a neat diagram explain the voltage divider biasing method for JFET. 8

8


- (b) The JFET shown has  $I_{DSS} = 6 \text{ mA}$  and  $V_p = -3 \text{ V}$ . Calculate :

(i)  $I_{DSQ}$

(ii)  $V_{DSQ}$

(iii)  $V_{GSQ}$



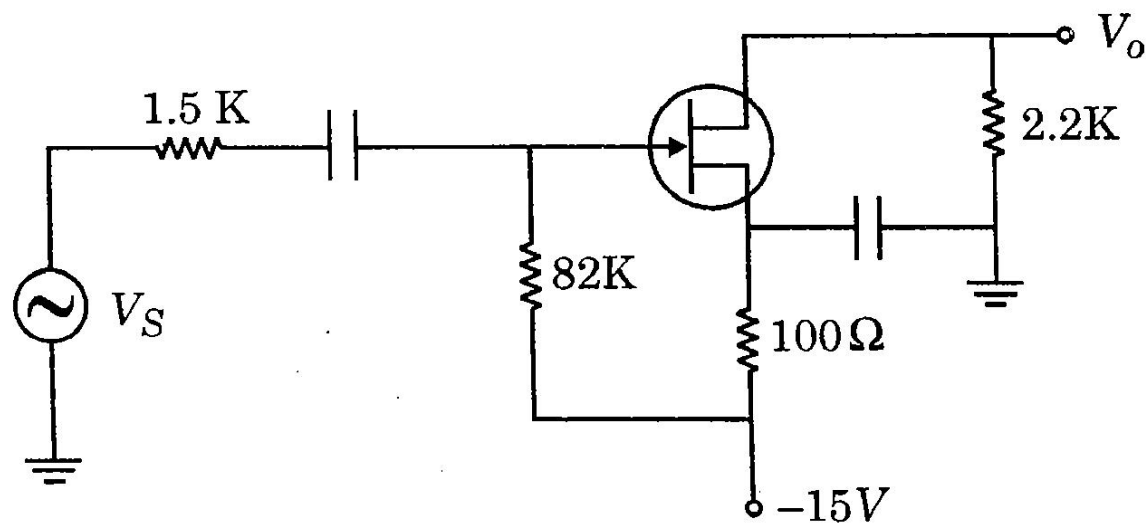

8

OR

- 4 (a) Explain the construction characteristics of a N-channel enhancement MOSFET.

8

- (b) Explain the working of FET as a voltage variable resistor (VVR).

8

- 5 (a) Deduce expressions for  $A_v$ ,  $A_i$ ,  $R_i$ ,  $R_o$ ,  $A_{vs}$  and  $A_{IS}$  in a CE BJT amplifier in terms of h-parameters.

10

- (b) State and explain Miller's theorem.

6


OR

- 5 (a) Write short notes on :

- (i) Bootstrapping  
(ii) Darlington Emitter follower.

8

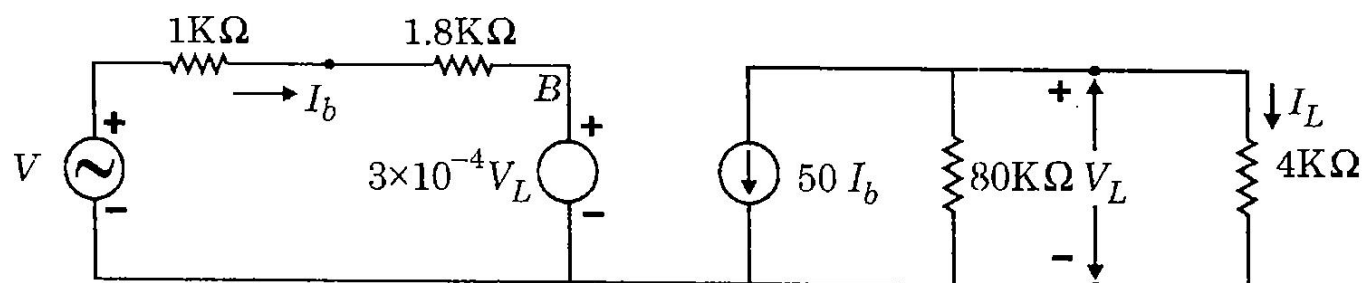- (b) In the fig shown, calculate current gain and voltage gain.



8

