

3E1483

Roll No. : _____

Total Printed Pages : 4

3E1483

B.Tech. (Sem. III) (Main/Back) Examination, February - 2010
Electrical Engineering
(3EE3 Circuit Analysis - I)

Time : 3 Hours]

[Total Marks : 80

[Min. Passing Marks : 24


Attempt overall **five** questions in all. Schematic diagrams must be shown wherever necessary. Any data you feel missing may suitably be assumed and stated clearly.

Use of following supporting material is permitted during examination.
(Mentioned in form No. 205)

1. _____ Nil _____

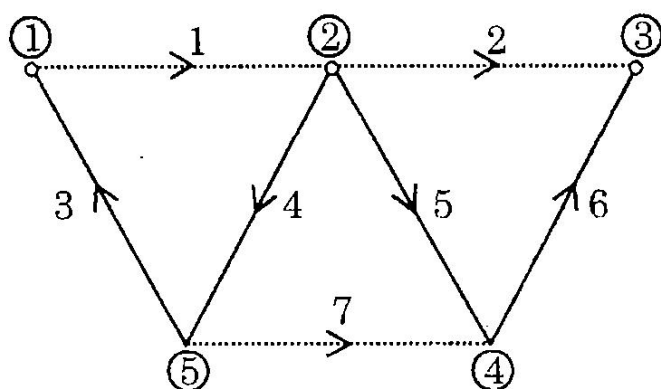2. _____ Nil _____

- 1 (a) A graph is shown in Fig. below. Find the tie-set and cut set matrices and obtain the KCL and KVL equations.




8

- (b) Deduce the expression for quality factor of a coil L with effective internal resistance R , connected to a sinusoidal voltage source $V_m \sin wt$.

8

OR

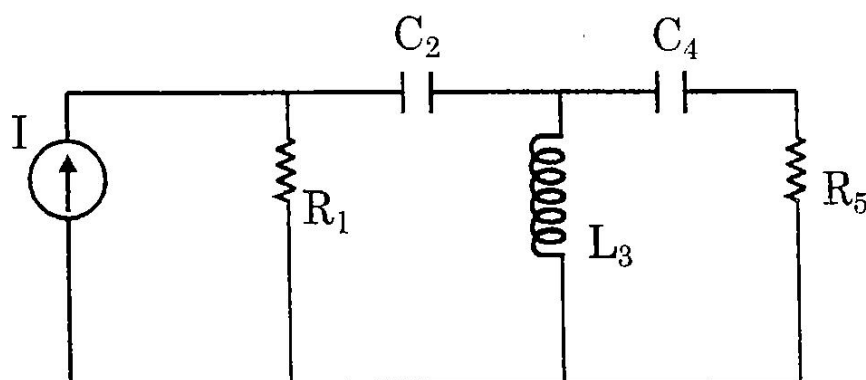- 1 (a) Draw the dual of the network shown below.



8

3E1483]




1

[Contd...

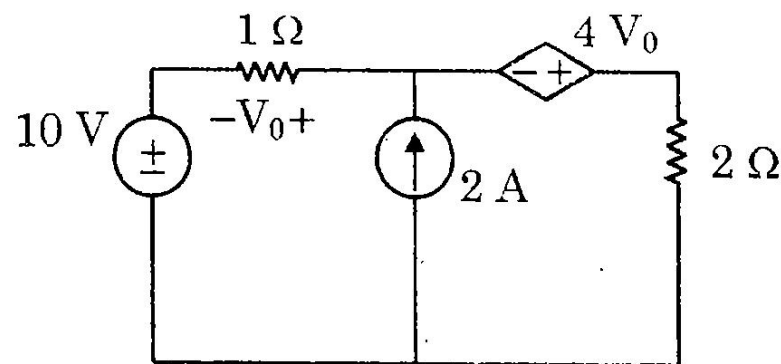- (b) A 220 V, 100 Hz a.c. source supplies a series RLC circuit with a capacitor and a coil. If the coil has $50 \text{ m}\Omega$ resistance and 5 mH inductance, find at a resonance frequency of 100 Hz, what is the value of capacitor? Also calculate the Q factor and half power frequencies of the circuit.

8

- 2 (a) Find the power loss in 2Ω resistor using Thevenin's theorem in Fig. below.




8

- (b) State and explain for maximum power transfer theorem that power transfer from a d.c. source network to a resistive network is maximum when the internal resistance of the d.c. source network is equal to the load resistance.

8

OR

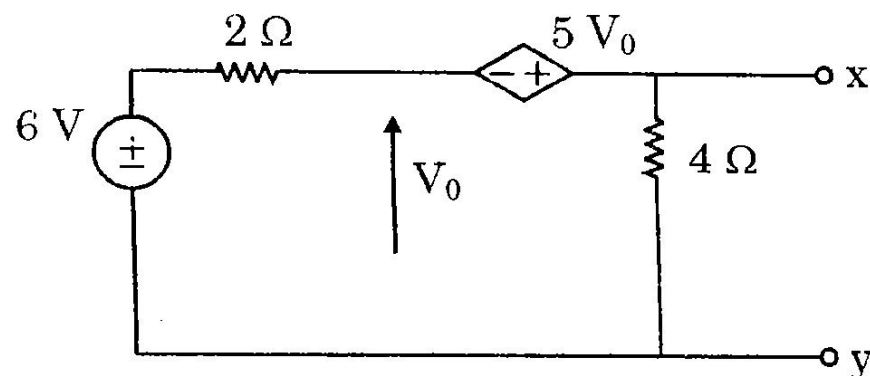- 2 (a) Find Norton's equivalent of the circuit shown below at the left of xy terminals.



8

- (b) State and explain for Tellegen's theorem that the sum of power delivered to a closed network is zero.

8

- 3 (a) A three phase 220 V supply is applied to balance delta connected three phase load. The phase current being $I_{ab} = 10 \angle -30^\circ \text{ A}$, find I_a . Compute the total power received by delta load. Find the value of the resistance portion of the phase impedance.

8



- (b) A three phase 400 V load has a power factor of 0.4. Two wattmeters are connected to measure the power. If the input power be 10 kW, find the reading of each instrument.

8

OR


- 3 (a) A 3 phase star connected system with 400 V (L-L) is connected to a three loads = $25 \angle 0^\circ$, $11 \angle -20^\circ$ and $15 \angle 10^\circ$ ohm (also connected in star). Find the line current, power and current in the neutral of the system.

8

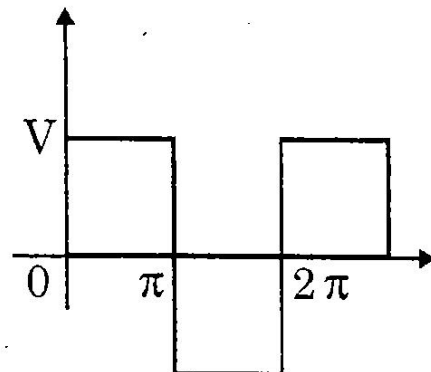- (b) a 100 kVA, 0.8 P.F. (lag) load runs in parallel to a 150 kW, 0.95 lead power factor load and the combination runs in parallel with 300 kVA, 250 kVar inductive load. Determine the complex power of the three loads.

8

- 4 (a) A square waveform is shown below. Obtain the Fourier series.



8


- (b) Explain the different kinds of symmetry in non-sinusoidal waves.

8

OR

- 4 (a) Find the Fourier series of the function shown in fig. below and is represented by
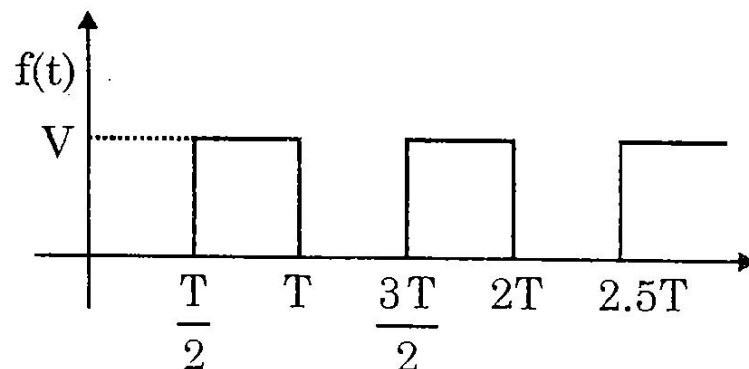
$$f(t) = \begin{cases} 0 & \text{for } 0 < t < \frac{T}{2} \\ A & \text{for } \frac{T}{2} < t < T \end{cases}$$




8



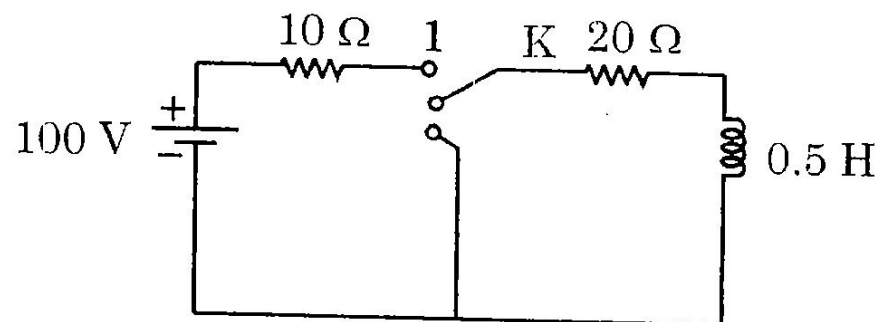- (b) Explain and derive the power relationship in non-sinusoidal waves with non-sinusoidal voltage and current. 8

- 5 (a) In fig. below, switch K is kept first at position 1 and steady state condition is reached. At $t=0$, the switch is moved to position 2. Find the current in both the cases. 8



- (b) Derive initial and final value theorems. 8

OR 8

- 5 (a) A 50 Hz, 400 V (peak value) sinusoidal voltage is applied at $t=0$ to a series R-L circuit having resistance $5\ \Omega$ and inductance $0.2\ \text{H}$. Obtain an expression of current at any instant t . Calculate the value of the transient current $0.1\ \text{sec}$. after switching on. 8

- (b) An impulse function is given by $s(t-t_1)$. Obtain its Laplace transform. 8

